

SIMULATION AND IMPLEMENTATION OF SEQUENTIAL LOGIC CIRCUITS

AIM:


To simulate and synthesis SR, JK, T, D - FLIPFLOP, COUNTER DESIGN using Xilinx ISE.

APPARATUS REQUIRED:

Xilinx 14.7 Spartan6 FPGA

LOGIC DIAGRAM:

SR FLIPFLOP:

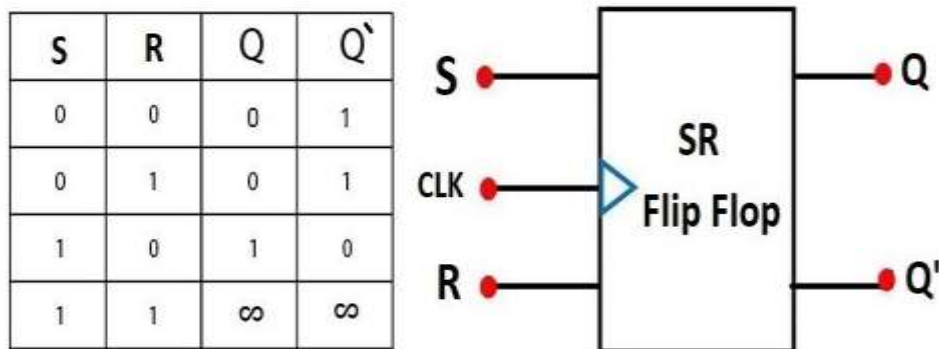

VERILOG CODE:

```
module srff(clk,rst,s,r,q);  
  
input clk,rst,s,r;  
  
output reg q;  
  
always @(posedge clk)  
  
begin  
  
if(rst)  
  
q<=1'b0;  
  
else  
  
begin  
  
case({s,r})
```

```

2'b00:q<=q;

2'b01:q<=1'b0;

2'b10:q<=1'b1;

2'b11:q<=1'bx;

default:q<=1'bx;

endcase


end

end


endmodule

```

OUTPUT:

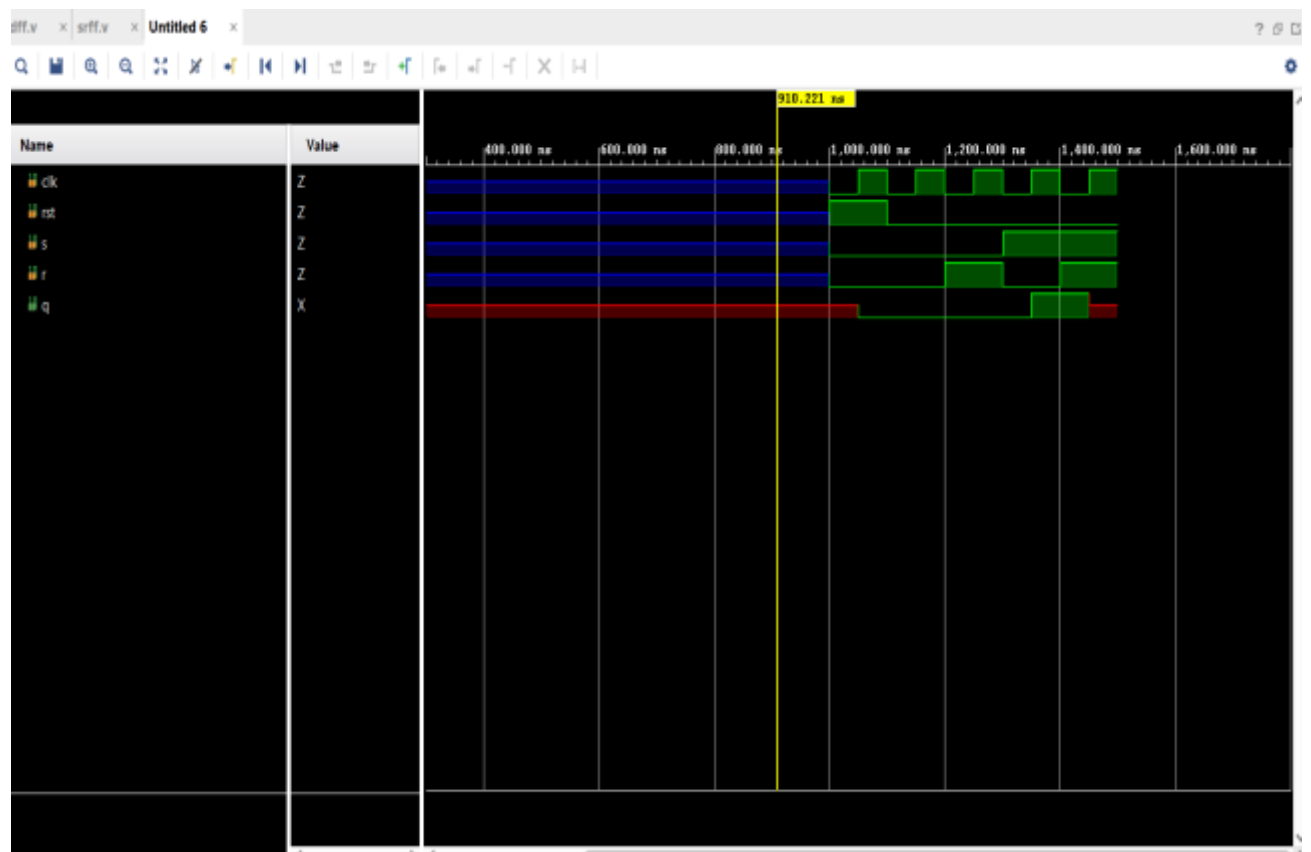

JK FLIPFLOP:

 

Truth Table

J	K	Q_N	Q_{N+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

VERILOG CODE:

```
module jkff(clk,rst,j,k,q);
```

```
input clk,rst,j,k;
```

```
output reg q;
```

```
always @(posedge clk)
```

```
begin
```

```
if(rst)
```

```
q<=1'b0;
```

```
else
```

```
begin
```

```
case({j,k})
```

```
2'b00:q<=q;
```

```
2'b01:q<=1'b0;
```

```
2'b10:q<=1'b1;
```

```
2'b11:q<=~q;
```

```
default:q<=1'bx;
```


```
endcase
```

```
end
```


```
end
```

```
endmodule
```

OUTPUT:

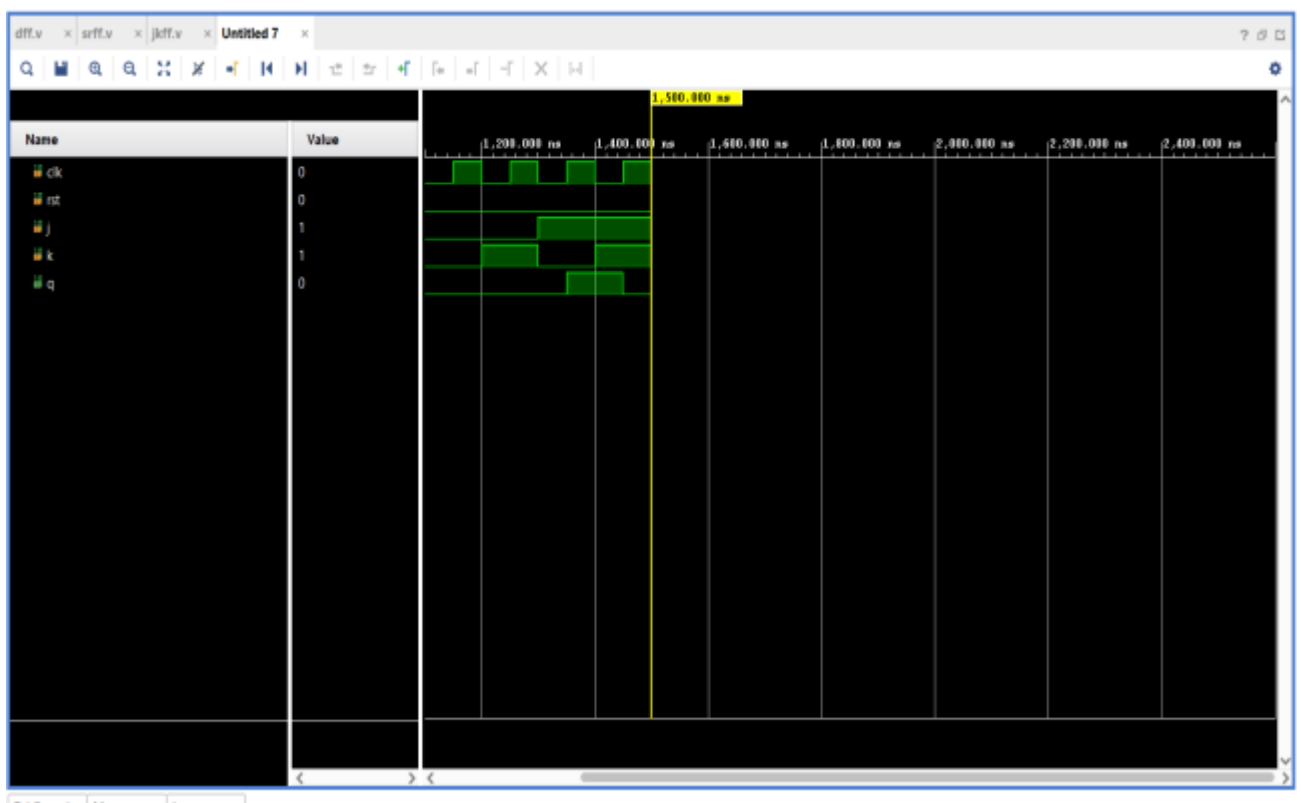

T FLIPFLOP:

 


T	Q	Q'
0	0	0
1	0	1
0	1	0
1	1	0


VERILOG CODE:

```
module tff(clk,rst,t,q);  
input clk,rst,t;  
output reg q;  
always @(posedge clk)  
begin  
    if(rst)  
        q<=0;  
    else if(t)  
        q<=~q;  
    else  
        q<=q;  
    end  
endmodule
```

OUTPUT:

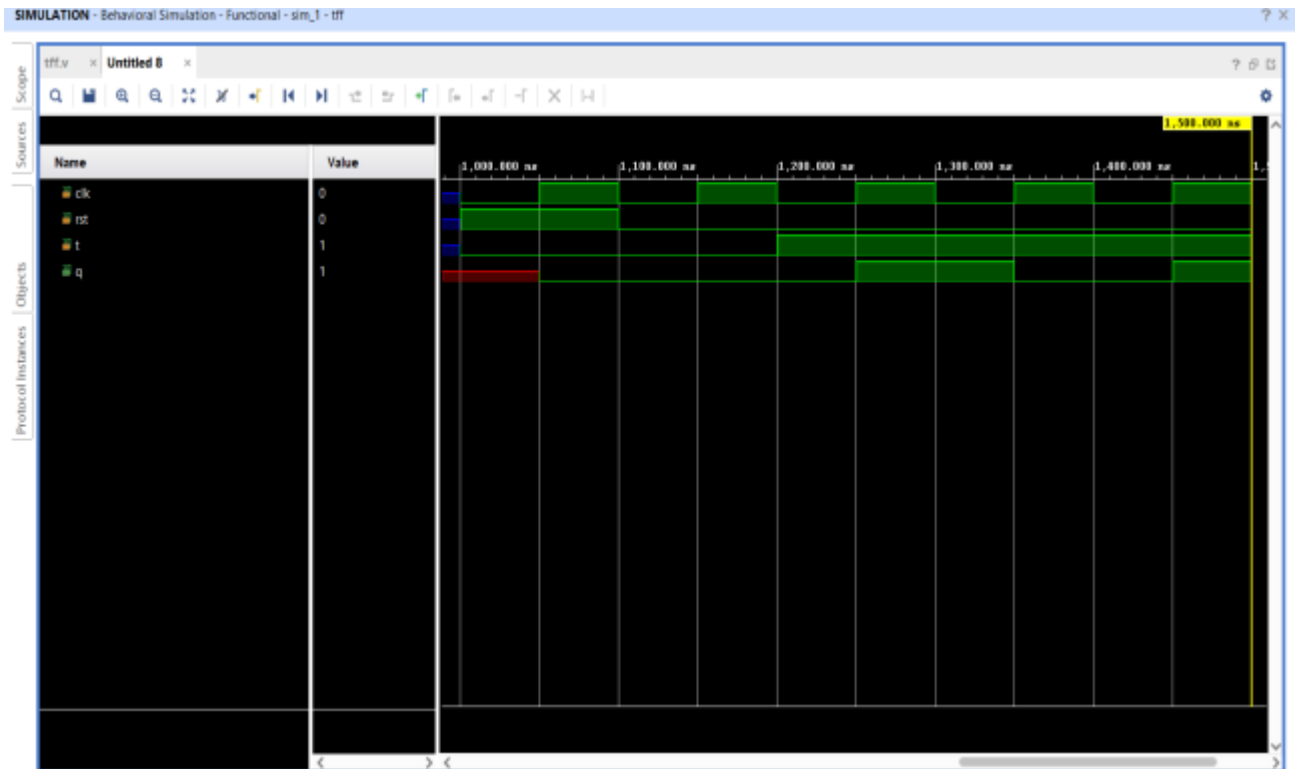

D FLIPFLOP:

 

C	D	Q	
0	x	Q_0	No change
1	0	0	Reset
1	1	1	Set

VERILOG CODE:

```
module dff(d,clk,rst,q);
```

```
input d,clk,rst;
```

```
output reg q;
```

```
always @(posedge clk)
```

```
begin
```

```
if(rst)
```

```
    q <= 1'b0;
```


```
else
```

```
    q <= d;
```

```
end
```

```
endmodule
```

OUTPUT:

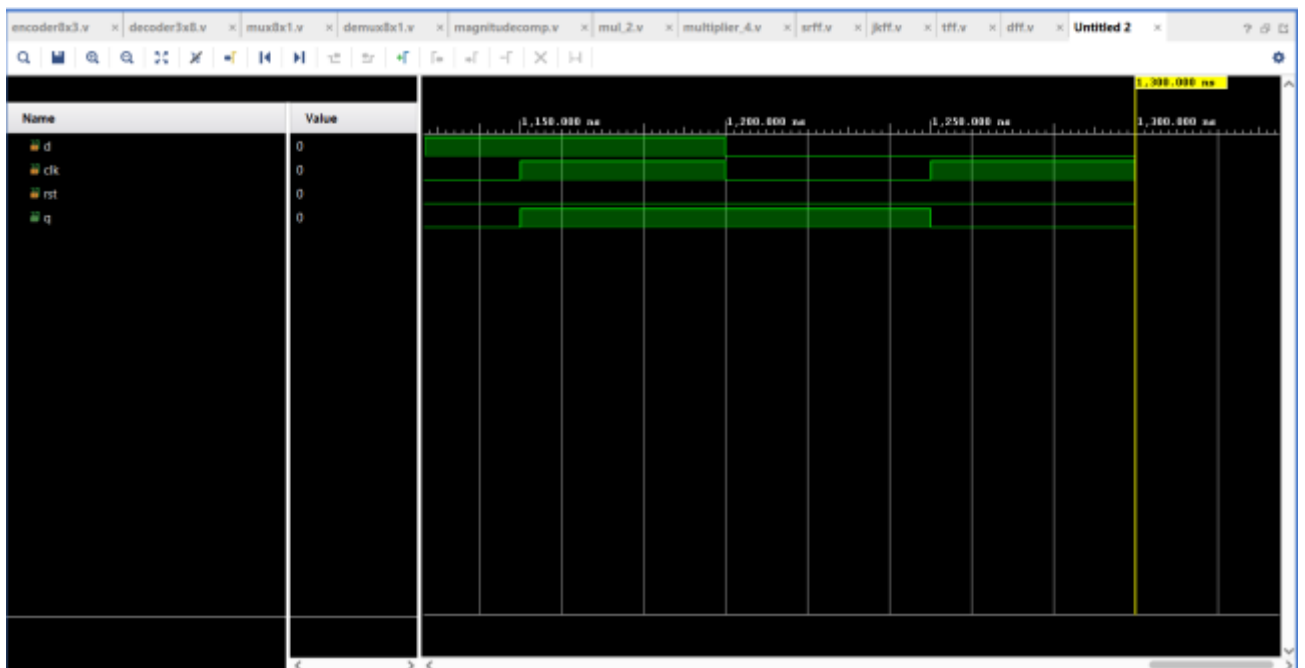

COUNTER

MOD10COUNTER:

VERILOG CODE:

```
module mod10counter(clk,rst,count);
```

```
input clk,rst;
```

```
output[3:0]count;
```

```
reg[3:0]count;
```

```
always@(posedge clk)
```

```
begin
```

```
if(rst|count==4'b1001)
```

```
count<=4'b0;
```


```
else
```

```
count<=count+1;
```

```
end
```

```
endmodule
```

OUTPUT:

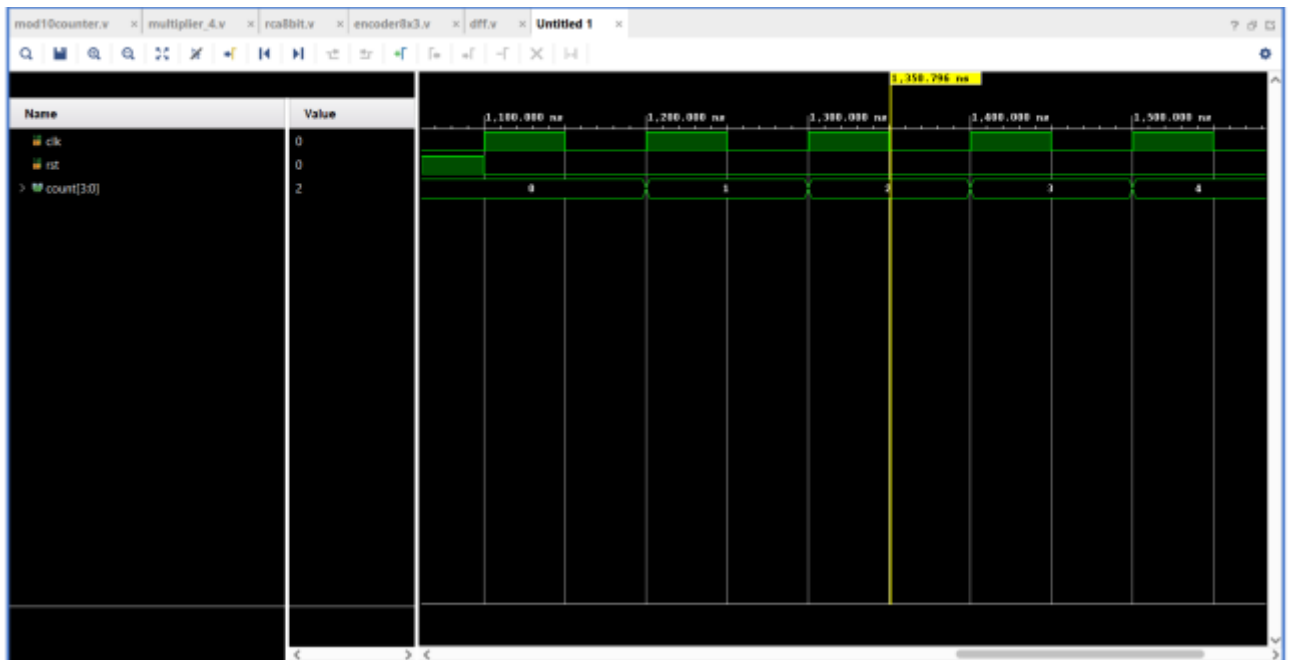

UPCOUNTER:


VERILOG CODE:

```

module upcounter(clk,rst,count);
input clk,rst;
output[3:0]count;
reg[3:0]count;
always@(posedge clk)
begin
if(rst)
count<=4'b0;
else
count<=count+1;
end
endmodule

```

OUTPUT:

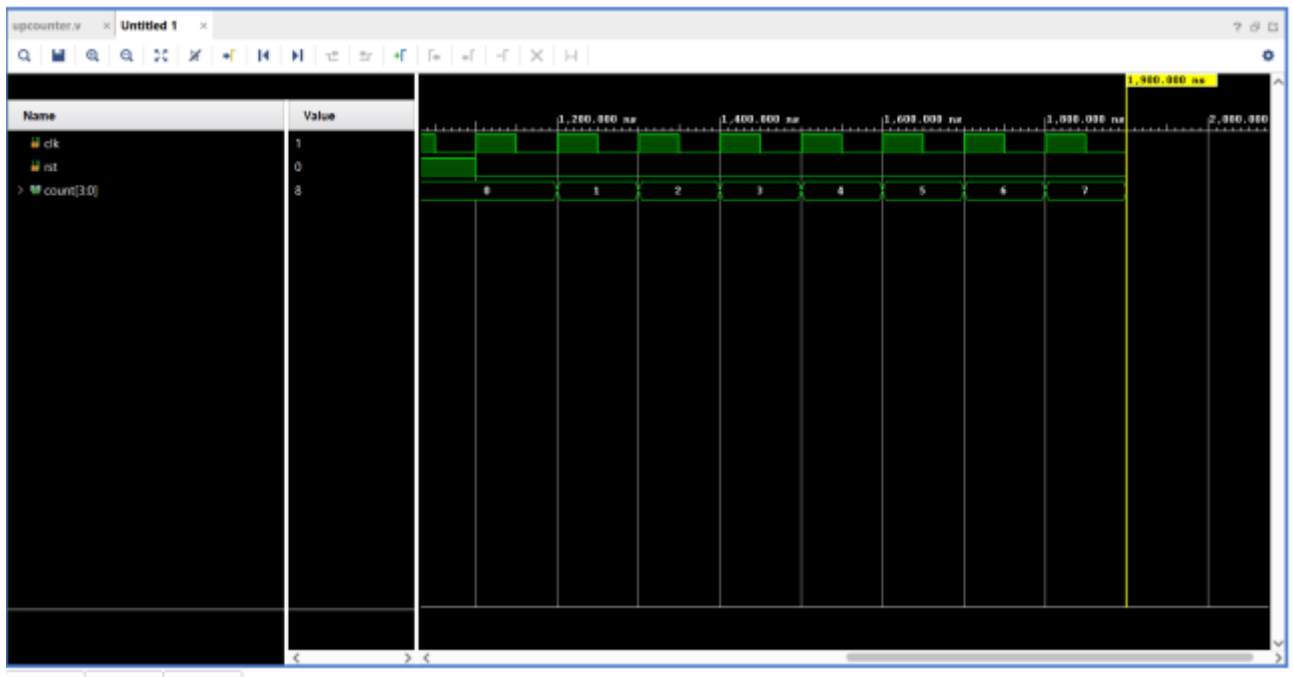


DOWN COUNTER:

VERILOG CODE:

```
module downcounter(clk,rst,count);
input clk,rst;
output[3:0]count;
reg[3:0]count;
always@(posedge clk)
begin
if(rst)
count<=4'b0;
else
count <=count-1;
end
endmodule
```

OUTPUT:

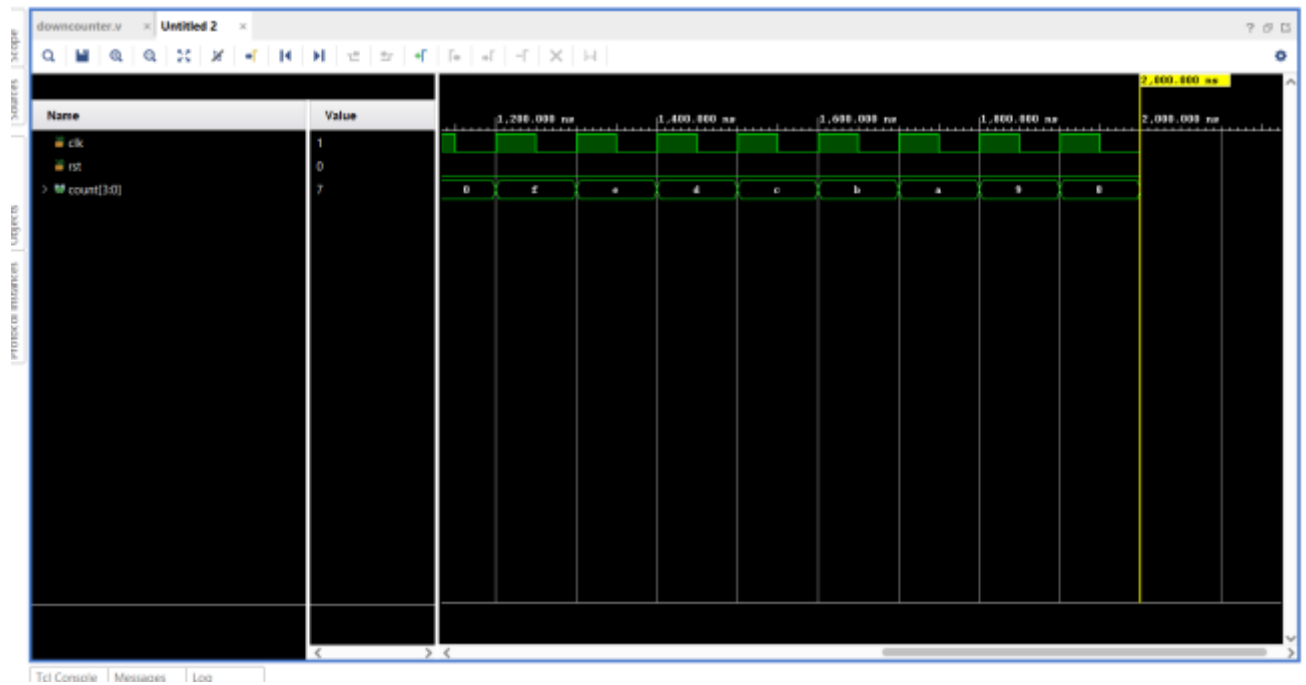

RIPPLE COUNTER:

VERILOG CODE:

```
module jkff(j,k,clock,reset,q,qb);  
input j,k,clock,reset;  
output reg q,qb;  
always@(negedge clock)  
begin  
case({reset,j,k})  
3'b100 :q=q;  
3'b101 :q=0;  
3'b110 :q=1;  
3'b111 :q=~q;  
default :q=0;  
endcase  
qb<=~q;
```

end

endmodule

```
module ripple_count(j,k,clock,reset,q,qb);
```

```
input j,k,clock,reset;
```

```
output wire [3:0]q,qb;
```

```
jkff JK1(j,k,clock,reset,q[0],qb[0]);
```

```
jkff JK2(j,k,q[0],reset,q[1],qb[1]);
```

```
jkff JK3(j,k,q[1],reset,q[2],qb[2]);
```

```
jkff JK4(j,k,q[2],reset,q[3],qb[3]);
```

endmodule

OUTPUT:

